

Hardware & Software for Information Technologies


Digital Sequential Circuits


NovaiMS, V.0.9 V.Lobo 2016

Sequential Circuits

Sistemas Lógicos (3)

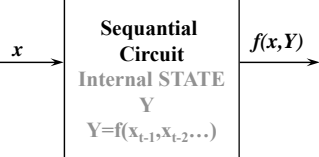- **Combinatory Circuits**
 - The output (in each point in time) depend **ONLY** on the inputs present at that moment.
 - They have no memory
- **Sequential Circuits**
 - The outputs depend on the **STATE** of the circuit
 - The **STATE** of the circuit depends on the previous inputs
 - They have **MEMORY**







1

Basic memory element

Sistemas Lógicos (3)

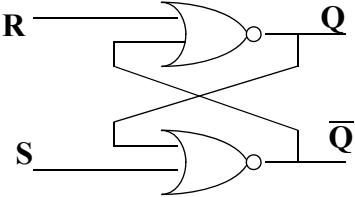- **How can we memorize a bit using only gates ?**
 - A pair of negations will maintain whatever state they have
 - It is not easy to change the state only with negations
- **S-R LATCH (Set-Reset)**
 - S (Set) input forces the output to 1
 - R (Reset) input forces the output to 0
 - 0



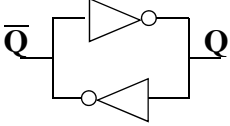

Can we describe a
SR LATCH
using thruth tables ?

2

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovalIMS, V.0.9 V.Lobo 2016

Description of sequential circuits

Sistemas Lógicos (3)

- Truth tables
 - The PREVIOUS STATE is used as an input
 - We may simplify the truth table, specifying the output as a function of the previous state

S	R	Q	$Q_{(t+1)}$
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	x
1	1	1	x

S	R	$Q_{(t+1)}$
0	0	Q
0	1	0
1	0	1
1	1	x

S,R	00	01	11	10
Q				
0	0	0	x	1
1	1	0	x	1

3

Description of sequential circuits

Sistemas Lógicos (3)

- Temporal diagrams
 - Show the *behaviour in time* of the circuits when they receive a given input
 - They do not define completely the behavior of a circuit ! (just the behavior to a PARTICULAR input)

Inputs, or forced signals

S

R

Response

Q

Condição inicial

Moments in time when transitions may occur

4

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovaisMS, V.0.9 V.Lobo 2016

Descriptions of Sequential circuits

Sistemas Lógicos (3)

- **Asynchronous circuits**

- As soon as the inputs change, the outputs may change immediately
- They can be very fast, but are not (yet) used much, because they are difficult to design and have problems with "critical runs"
 - Promising future, as discussed in Proceedings of the IEEE, February 1999

- **Synchronous circuits**

- There is synchronizing signal (called CLOCK) that regulates when transitions may occur
- There ONLY are transitions on the CLOCK EDGES
- In temporal diagrams we only need to analyse what happens in clock edges.
- The NEXT STATE is a function of what is present BEFORE the clock edge!
- After a CLK edge, where changes may occur, there is a "relaxation time" where changes will take place internally, and after they all stabilize, a new clock edge may occur. This limits the maximum speed.
- These are by far the most common circuits !


5

SR Latches

Sistemas Lógicos (3)

- **In the TTL family**

- 74279

 


74279

Nota: Todas as entradas são activas a 0

- **GATED LATCH**

 - Have an ENABLE input
- When ENABLE = 0, they keep the previous state. When ENABLE=1 it reacts to the R and S inputs.



6

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovaiMS, V.0.9 V.Lobo 2016

D type LATCH

Sistemas Lógicos (3)

- They have only one signal input D (from DELAY), and one enable signal.
- It is the basic MEMORY ELEMENT
 - The output is always available.
 - EN=1 ⇒ Store internally what is in the input
 - EN=0 ⇒ Keep what was stored previously

74373 has 8 Latches

7

FLIP-FLOPS

Sistemas Lógicos (3)

- FLIP-FLOP
 - Only changes it's outputs when a CLOCK edge occurs
 - Only one of the edges (RISING edge of the clock, or FALLING edge) leads to possible changes of the output.
- EDGE TRIGGERED FLIP-FLOP
 - Are sensitive to inputs in the moment just before the CLK edge
 - The "sensitivity window" is very narrow

▶ means
Edge-Triggered

8

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovaisIMS, V.0.9 V.Lobo 2016

Edge-Triggered Flip-Flop

Sistemas Lógicos (3)

- A flip-flop may have *Asynchronous inputs*, that act independaly from the CLK
 - CLEAR - forces the output to 0
 - PRESET - forces the output to 1

- They are normally used to provoque RESETs or impose special conditions (initial states, for example)

9

Other implementations

Sistemas Lógicos (3)

An Edge-Triggered FLIP-FLOP

RS LATCH
(using only two transistors)

- The way a circuit is physically implemented can vary considerably...

10

Hardware & Software for Information Technologies

Digital Sequential Circuits


NovaisMS, V.0.9 V.Lobo 2016

Flip-flops according to inputs: D,RS,JK,T


Sistemas Lógicos (3)

- D Flip-flops (delay)**
 - Memorizam e atrasam a entrada


D	Q
0	0
1	1

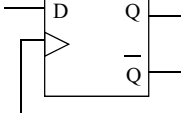
- RS Flip-flops (Set-Reset)**
 - São "ligados" e "desligados" por S e R


S	R	Q
0	0	Q
0	1	0
1	0	1
1	1	?

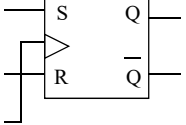
- JK Flip-Flops**
 - Quase iguais aos RS, mas resolvem a ambiguidade de R=S=1, fazendo neste caso um *TOGGLE* (invertendo o estado anterior)
 - O J faz Set, e o K faz Reset
 - Os mais usados na prática

J	K	Q
0	0	Q
0	1	0
1	0	1
1	1	\bar{Q}

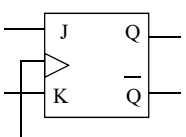
- T Flip-Flops (Toggle)**
 - Invertem o estado quando a entrada é 1

T	Q
0	Q
1	\bar{Q}

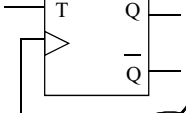


11

Master-Slave FLIP-FLOP

Sistemas Lógicos (3)

- Memoriza o que acontece quando o CLK está activo, mas só produz efeitos quando vem o flanco
- Tem uma concepção mais simples que os Edge-Triggered
- É composto por dois LATCHES em cadeia
 - Quando um está "transparente", o outro está "fechado"
 - Nunca há um caminho directo entre a entrada e saída
 - O Primeiro (Mestre) está ligado à entrada, e fornece dados ao Segundo (o Escravo)
- Tem "1's catching"
 - "Apanha" os picos

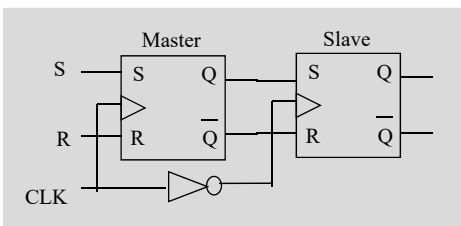

12

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovaisIMS, V.0.9 V.Lobo 2016

Simple Problems

Sistemas Lógicos (3)




- In na automobile Num automóvel, um dos pisca-piscas tem uma frequência de 2Hz. Pretende-se diminuir essa frequência para 0,5Hz. Projecte o circuito diminui a frequência do pisca-pisca.
- Pretende-se desenhar um alarme contra ladrões, que tenha uns sensores (por hipótese uns feixes de laser infra-vermelho) que enviam um sinal 1 quando não está ninguém presente, e 0 quando está (quando está alguém presente o feixe é interrompido). Existem 4 desses sensores, e quando qualquer um deles é activado, o alarme deverá começar a tocar. O alarme só deverá parar quando alguém premir o botão de "reset" que se encontra na sua caixa. Projecte este sistema.
- Desenhe um sistema para actuar sobre semáforos que põe o semáforo encarnado quando recebe um 1 e verde quando recebe um 0. Nas transições de verde para vermelho, E VICEVERSA, deverá 2 segundos no laranja.

13

Flip-Flops – Time issues

Sistemas Lógicos (3)

- Os flip-flops podem ser sensíveis ao flanco *Ascendente* ou *Descendente* (neste caso representados com uma bola no sinal de relógio, que significa que este é negado internamente)
- Propagation Delay
 - Tempo entre o clock e a reacção do integrado
 - Pode ser diferente para transições H-L ou L-H
- Set-Up Time
 - Antecedência com que é necessário actuar nas entradas
- Hold Time
- Rise Time
- Pulse Width

   

14

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovaisIMS, V.0.9 V.Lobo 2016

Timers and clock generators

Sistemas Lógicos (3)

- Geradores de Clock ou *Multivibradores Astáveis*
 - Geram ondas quadradas com uma dada frequência
- Implementação com PORTAS LÓGICAS
 - Frequências muito altas
 - Muito pouco fiáveis, pois os tempos de atraso podem variar muito

$$T \cong 2 \times n \times t_{pd}$$

$$f \cong 1 / (2 \times n \times t_{pd})$$

$$\text{Frequência} = \frac{1}{\text{Período}}$$

5 gates com $t_{pd} = 9\text{ns} \Rightarrow f = 11\text{MHz}$

15

Temporizadores

Sistemas Lógicos (3)

- Com Circuitos RC e portas lógicas
 - Facilmente ajustáveis
 - Pouco precisos (dependentes das tolerâncias das resistências e condensadores)

$$f = k \frac{1}{2RC}$$

- Com Cristais
 - Muito precisos
 - Só para frequências razoavelmente altas
 - Normalmente usam-se integrados dedicados para gerar o clock a partir de um cristal de quartzo

16

Hardware & Software for Information Technologies



Digital Sequential Circuits


NovaisIMS, V.0.9 V.Lobo 2016

Temporizadores Monoestáveis

Sistemas Lógicos (3)

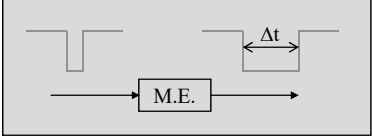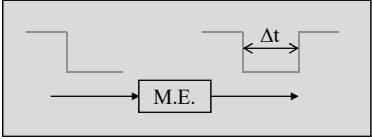- **Mono-estáveis**
 - Também chamados "one-shot"
 - Geram pulsos de largura fixa
 - Podem ser usados para
 - Gerar atrasos fixos
 - "Rectificar" picos





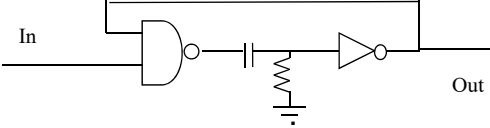17

Integrados para temporizadores dedicados

Sistemas Lógicos (3)

- **555**
 - Integrado muito flexível para circuitos temporizadores
 - Pode ser usado como monoestável ou gerador de clock
 - O "duty-cycle" pode ser regulado
 - É muito usado, e há bastantes "clones".
 - Esquema:
 - Pinout:

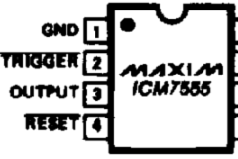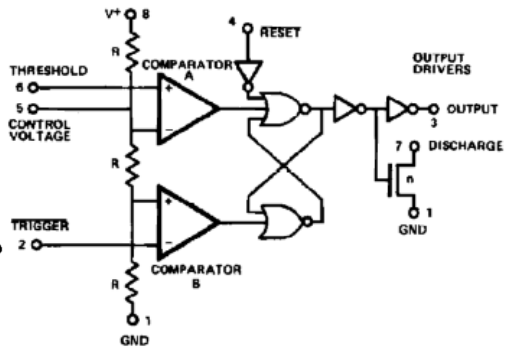18

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovaiMS, V.0.9 V.Lobo 2016

Integrated Circuits for clock generation

Sistemas Lógicos (3)

- Typical mountings for the 555

A) 50% duty-cycle Clock
 $f = 1 / (1,4 RC)$

B) Variable duty-cycle Clock
 $f = 1,46 / (Ra + 2Rb) C$
 $d = Rb / (Ra + 2Rb)$

C) Monostable
 $T_{pulso} = 1,1 RC$

19

Other Clock Generators

Sistemas Lógicos (3)

- Texas Instruments CDCE706 and TICE906
 - Use only 1 crystal (or another clock signal)
 - Can generate 6 clock signals with different frequencies and duty-cycles
 - Programmable by software
 - Keeps programming in an EEPROM
 - (more information on <http://focus.ti.com/docs/prod/folders/print/cdce706.html>)

PW PACKAGE
(TOP VIEW)

FUNCTIONAL BLOCK DIAGRAM

20

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovalIMS, V.0.9 V.Lobo 2016

Schmitt-Triggers

Sistemas Lógicos (3)

- May receive analog signals, but output digital
 - Output has only 2 levels
 - They are used to *regenerate* digital signals

- They have a hysteresis cycle:
 - To go from 0 to 1 the signal has to be significantly high, but to go from 1 to 0 the signal has to be significantly low
 - They eliminate "Cross-over noise"

What types of problems can be solved by these circuits ?

21

Registers

Sistemas Lógicos (3)

- How can we store information that needs more than 1 bit?
 - Use a set of Flip-Flops
 - Some sort of ordering is necessary to organize the flip-flops (FF)
- Registers
 - Basically, a collection of Flip-flops
 - They differ in how data is LOADED into the flips-flops; how that data is available to be READ from the outside; and possibly how data is passed from one flip-flop to another.
- Parallel Load Registers
 - Data is input and output in parallel
 - Operations:
 - Parallel-in/Parallel-out

22

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovalIMS, V.0.9 V.Lobo 2016

Shift Register

Sistemas Lógicos (3)

- **Shift Register** (*Registro de deslocamento*)
 - They are *tapped delays*
 - They have a *Serial-in* input and a *Serial-out* output
 - Data (stored internally) is usually also available to be read in parallel
 - May be used for series to parallel conversions
 - Some registers can do *shift-right* or *shift-left* operations
- Application example
 - Ring counter
 - Detect a sequence of bits (for example morse code 00011000)

23

Multifunction Registers

Sistemas Lógicos (3)

- **Parallel-in/serial-out registers**
 - May be used for Parallel/Serial conversions
 - They have a control input that selects which operation will be done:
 - Shift data (in this case from left to right)
 - Load new data in parallel

24

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovalIMS, V.0.9 V.Lobo 2016

Counters

Sistemas Lógicos (3)

- **What is a counter ?**
 - A system that **CYCLES** through a series of **STATES**
 - Examples of sequences:
 - 0,1,2,3,,0,1,2,3,0,1,2,3...
 - 9,7,5,3,1,9,7,5,3...
 - Natural Binary Counter
 - Corresponds to the traditional idea of counter
 - Counts 0,1,2,3...(2ⁿ-1)
 - Ring counter
 - Counts 100,010,001...100,010....

- **Modulus of a counter**
 - Number of states before returning to the initial state

25

Ring Counter

Sistemas Lógicos (3)

- **N flip-flops, with only one set at 1 while others are 0**
- **The active flip-flop passes its "1" onto the next when the clock edge arrives**
 - It's a shift register with feedback from the last bit
- **N flip-flops ⇒ N different states**
- **Example of a ring counter with 4 bits**
 - Counting sequence:

1000	↶
0100	
0010	
0001	
1000	
0100	
⋮	
⋮	
⋮	

26

Hardware & Software for Information Technologies


Digital Sequential Circuits

NovaisMS, V.0.9 V.Lobo 2016

Johnson Counter

Sistemas Lógicos (3)

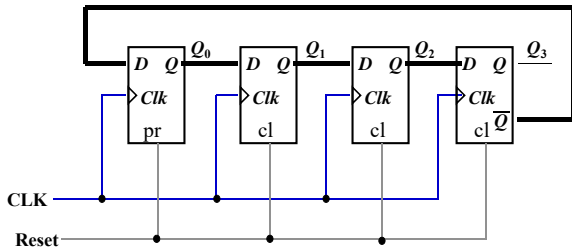- Similar to the ring counter, but the negation of the output is fed back to the input (instead of the output itself)
- N flip-flops $\Rightarrow 2N$ diferentes estados
- Example of a 4 bit Johnson counter
 - Counting Sequence



reset ↻

1000

1100

1110

1111

0111

0011

0001

0000

1000

1100

·


·

27

Synchronous Binary Counter (mod 2^n)

Sistemas Lógicos (3)

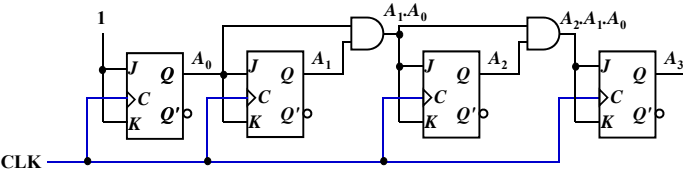- Counts in natural binary
 - The LSB (Least Significant Bit) always toggles
 - The more significant bits only toggle when all the previous bits are 1
- N flip-flops $\Rightarrow 2^N$ diferentes estados
- Example of a 4 bit synchronous binary counter
 - Counting Sequence



$A_3 A_2 A_1 A_0$

0000

0001

0010

0011

0100

0101

0110

0111

1000

1001

1010

1011

1100

1101

1110

1111

0000

0001

·

28

Hardware & Software for Information Technologies


Digital Sequential Circuits

NovalIMS, V.0.9 V.Lobo 2016


Asynchronous Binary Counter (ripple-mod 2^n)

Sistemas Lógicos (3)

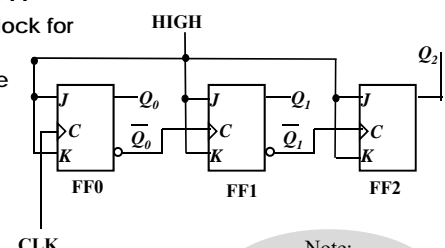- The clock is not common to all FF
 - The output of one flip-flop acts as clock for the next one
 - There are slight delays between the Flip-flops
- They are easier to build
 - They do not need external gates



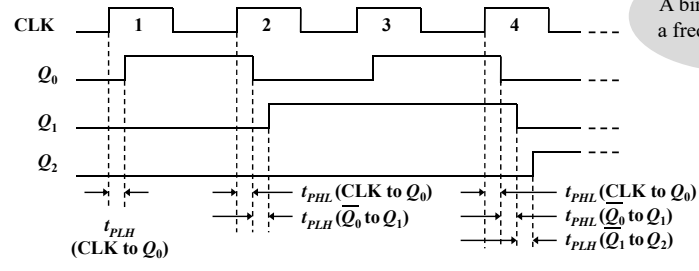Note: A binary counter is a frequency divider





29

Arbitrary modulus Binary Counter

Sistemas Lógicos (3)

- Key idea → Reset the counter before it finishes the natural cycle
 - Detect the first "unwanted" state, and force an asynchronous clear (reset)
 - Use AND gates to detect the unwanted state
 - The unwanted state will exist during a small peak

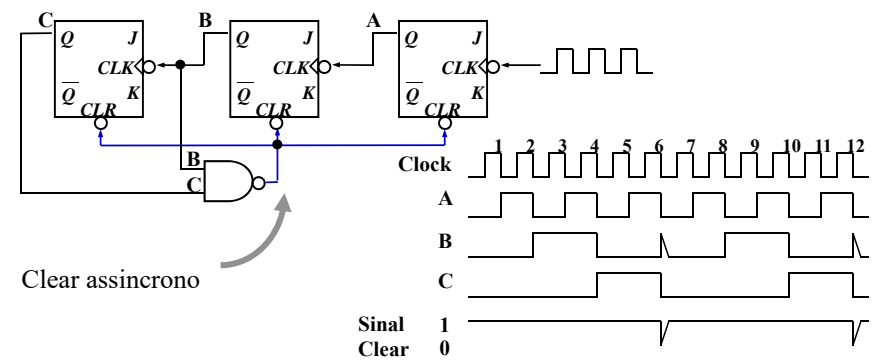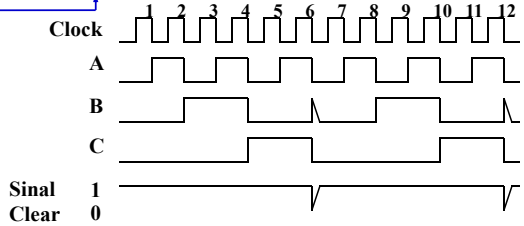30

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovalIMS, V.0.9 V.Lobo 2016

Examples modulus 6 counters

Sistemas Lógicos (3)

- 4 different ways of obtaining a modulus 6 counter with a modulus 16 binary counter with "parallel load" (synchronous) and clear (asynchronous)

(a) States 0,1,2,3,4,5.

(b) States 0,1,2,3,4,5.

(c) States 10,11,12,13,14,15.

(d) States 3,4,5,6,7,8.

33

Counters – Available digital circuits

Sistemas Lógicos (3)

- 7493
 - Asynchronous Binary Counter (ripple-counter) with 4 bits
 - 1st bit is independent from the others
 - It must be connected externally

7493	
Clk B	Clk A
R0(1)	NC
R0(2)	Qa
NC	Qd
VCC	GND
NC	Qb
NC	Qc

34

Hardware & Software for Information Technologies

Digital Sequential Circuits

NovalIMS, V.0.9 V.Lobo 2016

Contadores – Available devices

Sistemas Lógicos (3)

- **74163**
 - Synchronous 4 bit binary counter, with pre-load and enable
- **Others**
 - 74160 – Synchronous BCD counter
 - 74190 - Synchronous BCD up/down counter with pre-Load,

'ALS160B AND 'AS160 BINARY COUNTERS WITH DIRECT CLEAR

35

Counters – More complex devices

Sistemas Lógicos (3)

- **Maxim 7217**
 - Up/down 4 digit counter
 - Direct outputs for 7 segment displays (common cathod or anod and variable frequency)
 - Initial and final value are programmable
 - Output carry for cascading
 - Allows for very compact systems

BCD output of the data being displayed (doubles as input for programming initial and final values)

“feed” for the LEDs

36

Hardware & Software for Information Technologies

Digital Sequential Circuits


NovaisIMS, V.0.9 V.Lobo 2016

Counters – More complex devices

Sistemas Lógicos (3)

- 7250

 - Digitally programable timer (0-99)
- Unit delay defined by a RC circuit (thus, “tunable”)
- May generate delays from micro-seconds to days



Practical problem

For security reasons, we wish to prevent that more than 230 people get aboard one of boats that cross the Tagus river. In the entrance to the boats, there some rotating barriers that count how many people get in (sending a “1” pulse on the COUNT output each time someone passes). These barriers may be blocked by sending a “1” to the BLOCK input. The barrier should be blocked when 230 people have passed, and must only be unlocked when the boat leaves the pier. When it does, there is a sensor in the pier that sends a “1” pulse to it’s LEFT output.

Project this system

37